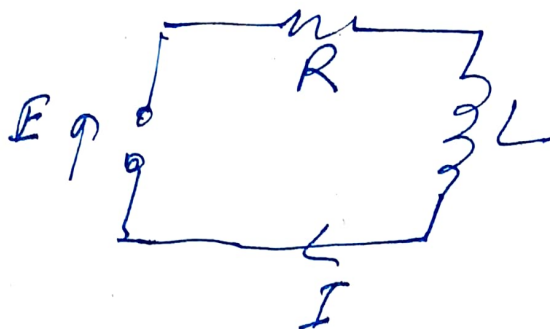


August 22, 2020 (2nd session)

Application to the 1st order Diff. equations.


Electrical Circuits

(R-L Circuit)



$$\frac{dI}{dt} + \frac{R}{L} I = \frac{E}{L}$$

(R-C circuit)

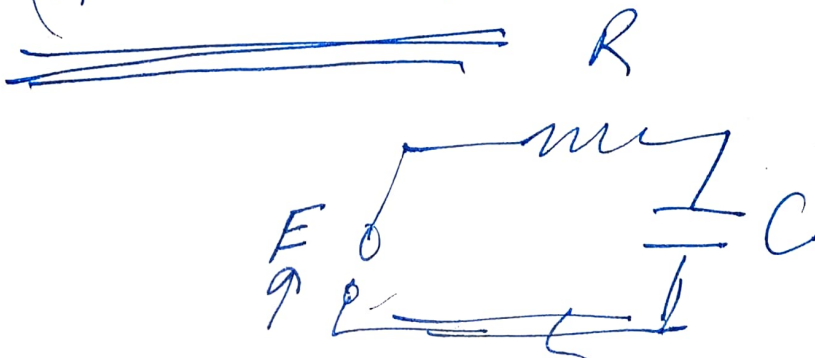

$$\frac{dq}{dt} + \frac{1}{RC} q = \frac{E}{R}$$

$$; \frac{dq}{dt} = I$$

(2)

Example

 :-

$$E = 5 \text{ volts}$$

$$R = 50 \, \Omega$$

$$L = 1 \text{ henry}$$

$$\frac{d}{dx} y + \underline{P(x)y} = \underline{Q(x)}$$

$$I \Big|_{t=0} = 0, \quad I \Big|_{t=t_1} = ?$$

The fundamental equation of
RL-circuit is:

$$\frac{d}{dt} I + \frac{R}{L} I = \frac{E}{L} \quad \text{--- (1)}$$

 \Rightarrow

$$\frac{d}{dt} I + \frac{50}{1} I = \frac{5}{1}$$

or

$$\frac{d}{dt} I + \underline{50} I = \underline{5} \quad \text{--- (2)}$$

This is a linear differential eq with
 $P = 50$ and $Q = 5$

$$\begin{aligned} \int P(x)dx &= \int 50 \cdot dx \quad (3) \\ I.F = e^{\int 50 \cdot dx} &= e^{50x} \\ &= e^{50t} \end{aligned}$$

The solution of the eq (2) is.

$$I \cdot (e^{50t}) = \int e^{50t} \cdot 5 \cdot dt + C$$

$$= \frac{1}{10} \int \underline{e^{50t} \cdot 50} \cdot dt + C$$

$$I(e^{50t}) = \frac{1}{10} e^{50t} + C \quad \text{Ans}$$

$$I = \frac{1}{10} + C e^{-50t} \quad (3)$$

at $t=0$, $I=0$

$$\text{Eq (3)} \Rightarrow 0 = \frac{1}{10} + C \cdot e^0$$

$$\boxed{-\frac{1}{10} = C}$$

Putting in Eq. (3)

$$\Rightarrow \boxed{\begin{array}{l} I_f = -\frac{1}{10} e^{-50t} + \frac{1}{10} \\ t_1 = t \end{array}}$$

Example 2

0
0—

$$E = 3 \sin 2t.$$

$$R = 10 \Omega$$

$$L \text{ ~~is~~ } = 0.5 \text{ henry.}$$

$$I_f = 6 \text{ amperes}$$

$$t=0$$

$$I_f = ?$$

$$t_1 = t$$

The governing eq. for RL-circuit

(5)

$$\frac{dI}{dt} + \frac{R}{L} I = \frac{E}{L}$$

$$\Rightarrow \frac{dI}{dt} + \frac{10}{0.5} I = \frac{3 \sin 2t}{0.5}$$

$$\text{or } \frac{dI}{dt} + \underline{20} I = \underline{6 \sin 2t} \quad \text{--- (1)}$$

$$\underline{P} = \int 20 \cdot dt \quad \therefore 20t$$

$$\Rightarrow I \cdot F = e \quad = e$$

The solution of eq. (1) is

$$I \left(\frac{20t}{e} \right) = \int \frac{20t}{e} \cdot 6 \sin 2t \cdot dt + C$$

$$I \left(\frac{20t}{e} \right) = 6 \int \frac{20t}{e} \cdot \sin 2t \cdot dt + C \quad \text{--- (2)}$$

$$P_1 = \int \frac{20t}{e} \cdot \sin 2t \cdot dt$$

$$= e^{\frac{20t(-\cos 2t)}{2}} - \int \left(\frac{-\cos 2t}{2} \right) e^{\frac{20t}{2}} \cdot 20 \cdot dt$$

$$P_1 = -\frac{1}{2} e^{20t} \cos 2t + 10 \int \frac{e^{20t} \cos 2t}{I} \cdot \frac{1}{I} dt$$

$$= -\frac{1}{2} e^{20t} \cos 2t + 10 \int \frac{e^{20t} \sin 2t}{2} - \int \frac{\sin 2t \cdot e^{20t}}{2} \cdot 20 dt$$

$$= -\frac{1}{2} e^{20t} \cos 2t + 10 \left[\frac{1}{2} e^{20t} \sin 2t - 10 \int e^{20t} \sin 2t \cdot dt \right]$$

or

$$P_1 = -\frac{1}{2} e^{20t} \cos 2t + 5 e^{20t} \sin 2t - 100 P_1$$

$$(101) P_1 = -\frac{1}{2} e^{20t} \cos 2t + 5 e^{20t} \sin 2t$$

$$P_1 = -\frac{1}{202} e^{20t} \cos 2t + \frac{5}{101} e^{20t} \sin 2t$$

$$P_1 = e^{20t} \left[-\frac{1}{202} \cos 2t + \frac{5}{101} \sin 2t \right]$$

using value of P_1 in eq. (2) (7)

$$\Rightarrow I(e^{20t}) = 6 \cdot \left[e^{20t} \left(-\frac{1}{202} \cos 2t + \frac{5}{101} \sin 2t \right) \right] + C$$

or

$$I(e^{20t}) = \left[-\frac{3}{101} \cos 2t + \frac{30}{101} \sin 2t \right] e^{20t} + C e^{20t}$$

$$\Rightarrow I = -\frac{3}{101} \cos 2t + \frac{30}{101} \sin 2t + C e^{-20t} \quad \text{L (2)}$$

at $t=0$, $I=6$

Eq. (2)

$$\Rightarrow 6 = -\frac{3}{101} (1) + 0 + C \cdot (1)$$

$$C = 6 + \frac{3}{101} = \frac{606+3}{101} = \frac{609}{101}$$

$$(2) \Rightarrow I = -\frac{3}{101} \cos 2t + \frac{30}{101} \sin 2t + \frac{609}{101} e^{-20t}$$